

Ερώτημα 1

Κώδικας:

Ln#	
1	LIBRARY ieee;
2	USE ieee.std_logic_1164.all;
3	
4	entity test_reg8 is
5	end test_reg8;
6	
7	architecture test_b of test_reg8 is
8	
9	signal D1: std_logic_vector(3 downto 0) := "0110";
10	signal Q1: std_logic_vector(3 downto 0);
11	signal R1: std_logic := '1';
12	signal C1: std_logic;
13	
14	component reg8 port(
15	D: IN STD_LOGIC_VECTOR(3 DOWNTO 0);
16	Resetn, Clock: IN STD_LOGIC;
17	Q: OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
18	
19	end component;
20	
21	begin
22	R8: reg8 PORT MAP (D=> D1, Q=> Q1, Resetn=>R1, Clock=> C1);
23	
24	Clock_process : PROCESS
25	BEGIN
26	C1 <= '0';
27	WAIT FOR 5 ps;
28	C1 <= '1';
29	WAIT FOR 5 ps;
30	END PROCESS;
31	
32	
33	Stimulus_process : PROCESS
34	BEGIN
35	
36	WAIT FOR 10 ps;
37	D1 <= "1110";
38	WAIT FOR 10 ps;
39	D1 <= "1010";
40	WAIT FOR 10 ps;
41	WAIT;
42	END PROCESS;
43	
44	END test_b;
45	

Wave



Κώδικας TestBench:


Ln#	
1	<code>LIBRARY ieee;</code>
2	<code>USE ieee.std_logic_1164.all;</code>
3	
4	<code>entity test_reg8 is</code>
5	<code>end test_reg8;</code>
6	
7	<code>architecture test_b of test_reg8 is</code>
8	
9	<code> signal D1: std_logic_vector(3 downto 0) := "0110";</code>
10	<code> signal Q1: std_logic_vector(3 downto 0);</code>
11	<code> signal R1: std_logic := '1';</code>
12	<code> signal C1: std_logic;</code>
13	<code> </code>
14	<code> component reg8 port(</code>
15	<code> D: IN STD_LOGIC_VECTOR(3 DOWNTO 0);</code>
16	<code> Resetn, Clock: IN STD_LOGIC;</code>
17	<code> Q: OUT STD_LOGIC_VECTOR(3 DOWNTO 0));</code>
18	
19	<code> end component;</code>
20	
21	<code>begin</code>
22	<code> R8: reg8 PORT MAP (D=> D1, Q=> Q1, Resetn=>R1, Clock=> C1);</code>
23	
24	<code>Clock_process : PROCESS</code>
25	<code> BEGIN</code>
26	<code> C1 <= '0';</code>
27	<code> WAIT FOR 5 ps;</code>
28	<code> C1 <= '1';</code>
29	<code> WAIT FOR 5 ps;</code>
30	<code> END PROCESS;</code>
31	
32	
33	<code> Stimulus_process : PROCESS</code>
34	<code> BEGIN</code>
35	
36	<code> WAIT FOR 10 ps;</code>
37	<code> D1 <= "1110";</code>
38	<code> WAIT FOR 10 ps;</code>
39	<code> D1 <= "1010";</code>
40	<code> WAIT FOR 10 ps;</code>
41	<code> WAIT;</code>
42	<code> END PROCESS;</code>
43	
44	<code>END test_b;</code>
45	

Ερώτημα 3

Κώδικας:

```
library ieee;
use ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
entity regfile is
  generic ( dw : natural := 4;
  size : natural := 4;
  adrw : natural := 2);
port ( A : in std_logic_vector(dw-1 downto 0);
  rAddr1: in std_logic_vector(adrw-1 downto 0);
  rAddr2: in std_logic_vector(adrw-1 downto 0);
  wAddr : in std_logic_vector(adrw-1 downto 0);
  we : in std_logic;
  clk : in std_logic;
  reset : in std_logic;
  B : out std_logic_vector(dw-1 downto 0);
  C : out std_logic_vector(dw-1 downto 0));
end regfile;
architecture behavioral of regfile is
  type regArray is array(0 to size-1) of std_logic_vector(dw-1 downto 0);
  signal regfile : regArray;
begin
  process(clk)
  begin
    if (clk'event and clk='0') then
      if we='1' then
        regfile(to_integer(unsigned(wAddr))) <= A;
      end if;
    end if;
  end process;
  C <= regfile(to_integer(unsigned(rAddr2)));
end behavioral;
```

Wave

 

Κώδικας TestBench:

```
library ieee;
use ieee.std_logic_1164.all;

entity regfile_ext_tb is
end regfile_ext_tb;

architecture behav of regfile_ext_tb is

component regfile_ext is
generic (
    dw: natural := 4;
    sz: natural := 4;
    addrw: natural := 2
);
port (
    a: in std_logic_vector(dw-1 downto 0);
    raddr1: in std_logic_vector(addrw-1 downto 0);
    raddr2: in std_logic_vector(addrw-1 downto 0);
    waddr: in std_logic_vector(addrw-1 downto 0);
    we: in std_logic;
    clk: in std_logic;
    rst: in std_logic;
    b: out std_logic_vector(dw-1 downto 0);
    c: out std_logic_vector(dw-1 downto 0)
);
end component;

signal s_dw: natural := 4;
signal s_sz: natural := 4;
signal s_addrw: natural := 2;
signal s_a: std_logic_vector(s_dw-1 downto 0);
signal s_raddr1: std_logic_vector(s_addrw-1 downto 0);
signal s_raddr2: std_logic_vector(s_addrw-1 downto 0);
signal s_waddr: std_logic_vector(s_addrw-1 downto 0);
signal s_we: std_logic;
signal s_clk: std_logic;
signal s_rst: std_logic;
signal s_b: std_logic_vector(s_dw-1 downto 0);
signal s_c: std_logic_vector(s_dw-1 downto 0);

begin
    uut: regfile_ext port map (
        a => s_a,
        raddr1 => s_raddr1,
        raddr2 => s_raddr2,
        waddr => s_waddr,
        we => s_we,
        clk => s_clk,
        rst => s_rst,
        b => s_b,
        c => s_c
    );
```

```

process begin
    s_we <= '1';
    s_clk <= '1';
    s_rst <= '1';
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '0';
    s_rst <= '0';
    s_raddr1 <= "00";
    s_raddr2 <= "00";
    s_waddr <= "00";
    s_a <= "0101";
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '1';
    s_rst <= '1';
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '0';
    s_rst <= '0';
    s_raddr1 <= "01";
    s_raddr2 <= "01";
    s_waddr <= "01";
    s_a <= "1010";
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '1';
    s_rst <= '1';
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '0';
    s_rst <= '0';
    s_raddr1 <= "10";
    s_raddr2 <= "10";
    s_waddr <= "10";
    s_a <= "0000";
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '1';
    s_rst <= '1';
    wait for 250 ns;

    s_we <= '1';
    s_clk <= '0';
    s_rst <= '0';
    s_raddr1 <= "11";
    s_raddr2 <= "11";
    s_waddr <= "11";
    s_a <= "1111";
    wait for 250 ns;
end process;
end behav;

```